


Squishy Logic

@SteveBattle

Squishy Circuits

- “Squishy circuits are a project from the **Playful Learning Lab** at the **University of St. Thomas**. The goal of the project is to design tools and activities which allow kids of all ages to create circuits and explore electronics using play dough.”
- <http://courseweb.stthomas.edu/apthomas/SquishyCircuits/>

Building a circuit

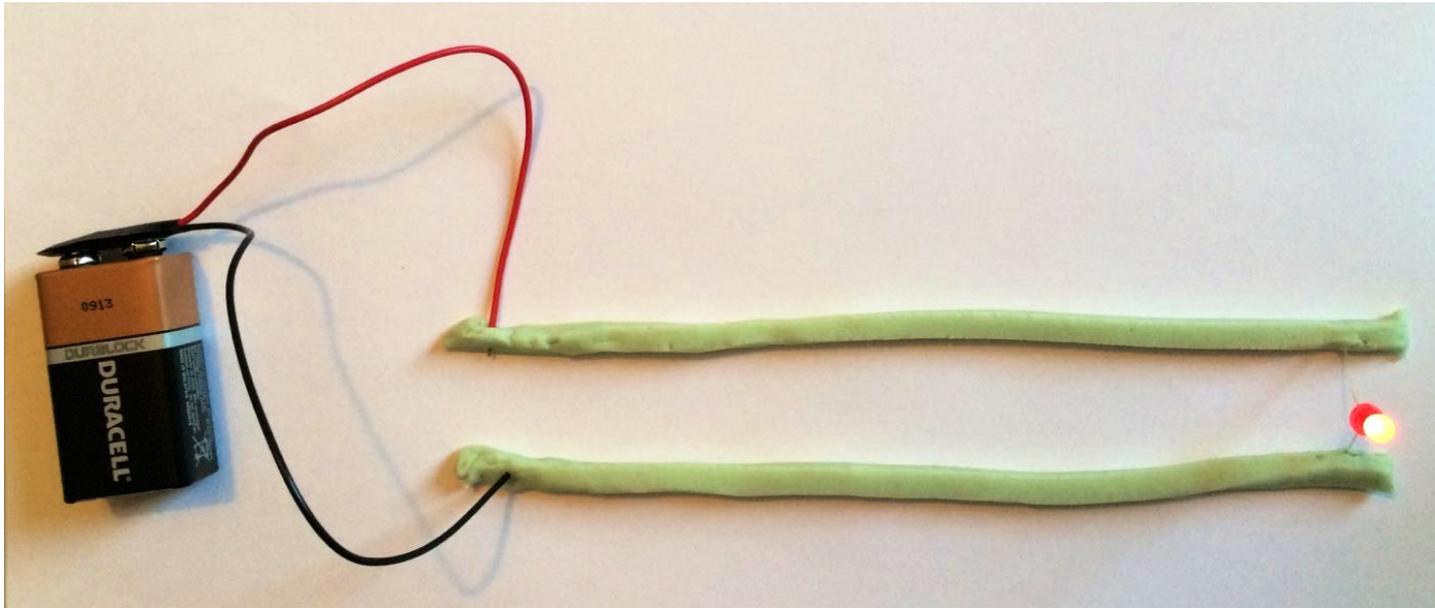

- 9V Battery (PP3).
- Light Emitting Diode (LED)
- The longer anode connects to +9V (red).
- The shorter *cathode* connects to 0V (black).
- The play dough is a *resistor*. Please don't connect the LED directly to the battery as this will release the magic smoke (bad).

Conductive Dough Recipe

Makes approximately 500g play-dough


- 1 cup water
- 1½ cups of flour
- ¼ cup of salt
- 3 tbsp. Cream of Tartar or 9 tbsp. lemon juice
- 1 tbsp. vegetable oil
- food colouring

Source: <http://courseweb.stthomas.edu/apthomas/SquishyCircuits/conductiveDough.htm>

Squish-tronics


Our mission is to rescue the squishbot from a maze. At each junction the robot's *squish-tronic* brain receives input and it has to make a decision to turn left or right.

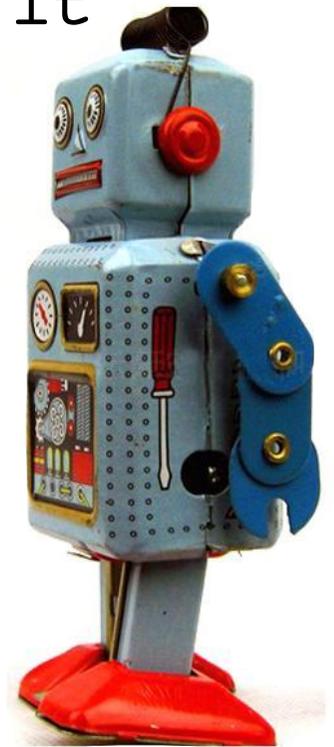- **Input:** The switch can be ON or OFF.
 - Representing **true/false** or **1/0**.
- **Output:** The LED lamp can be ON or OFF
 - Representing a **left** or **right** turn.





First Challenge

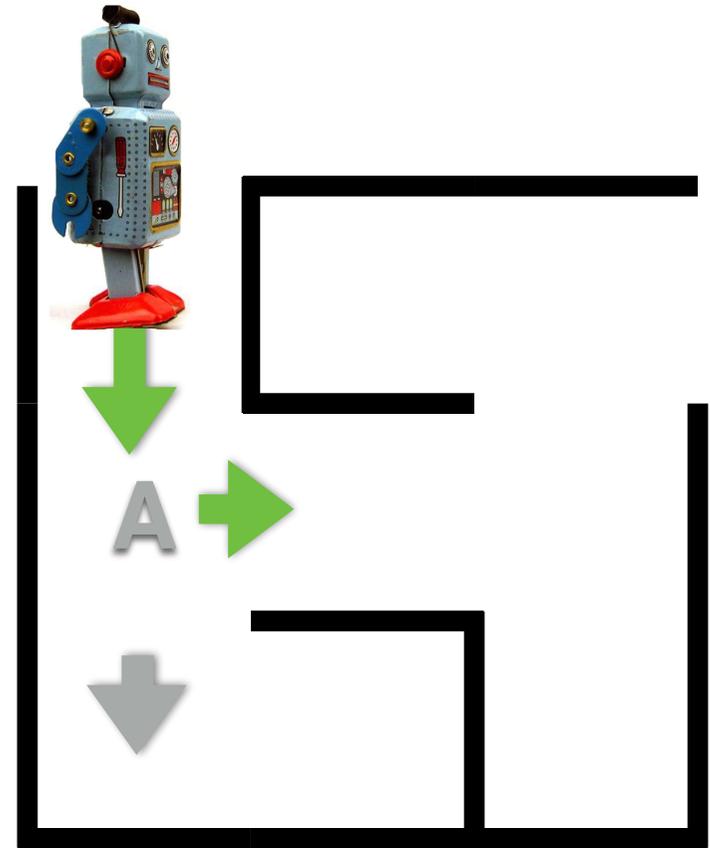- At the first junction the robot sees a sign 'A' on the wall.
- Instruct the robot to turn left (LED ON) if it sees input **A**.




Making a switch

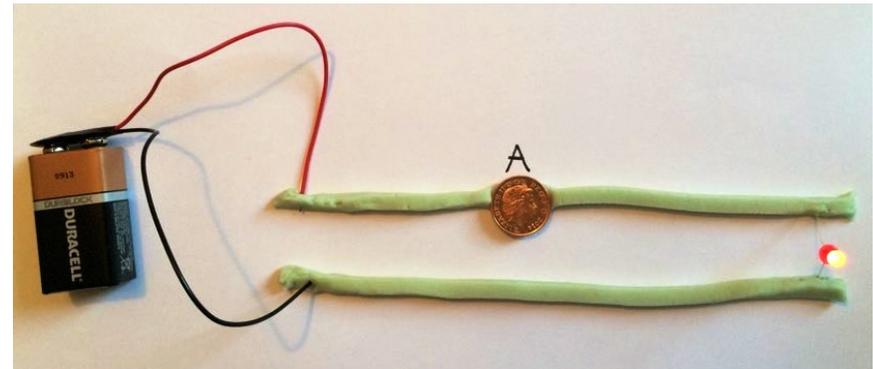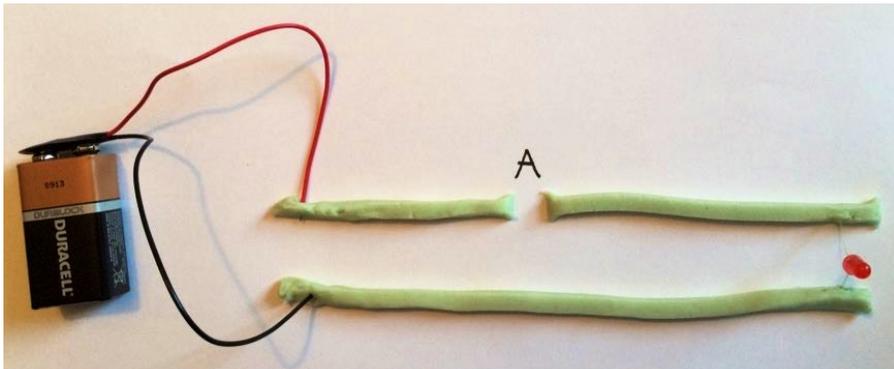- Cut a gap to break the circuit.
- Place a penny across the gap to make a switch.




Second Challenge

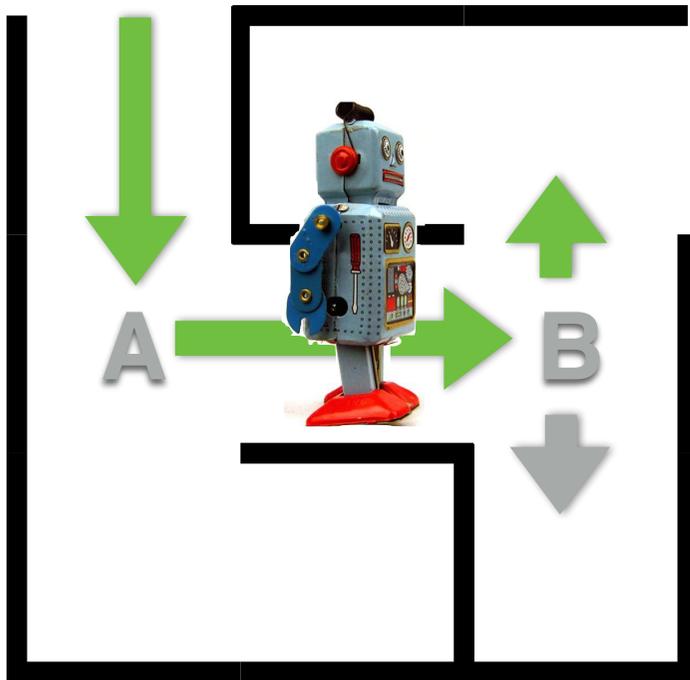- At the second junction the robot sees the sign 'B' on the wall.
- Instruct the robot to turn left (LED ON) if it sees either input **A**, **B**.







Turn left if:
A or B

Logical OR

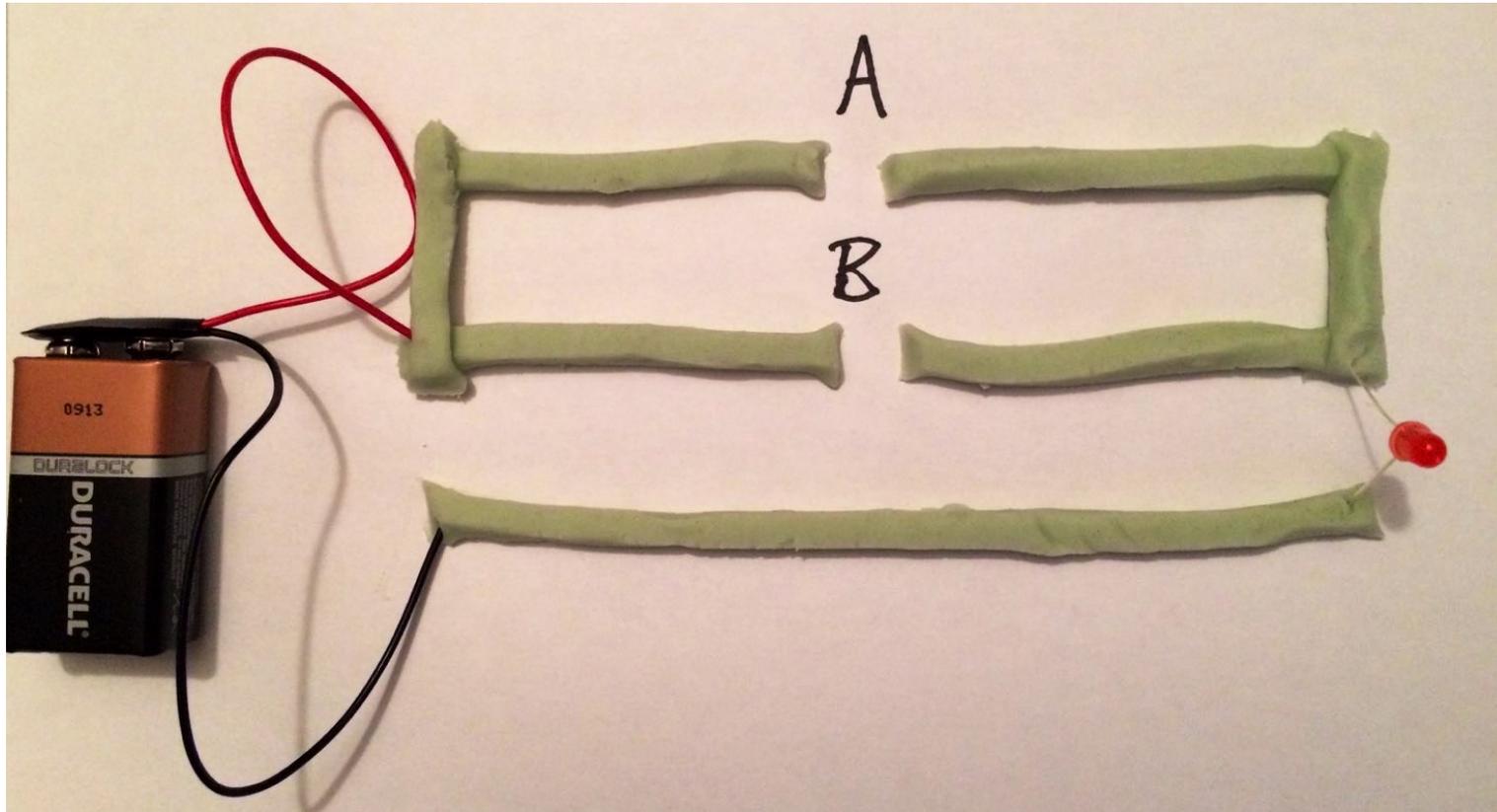

- The electrical current can follow either path.
- The switches are in parallel.


A or B

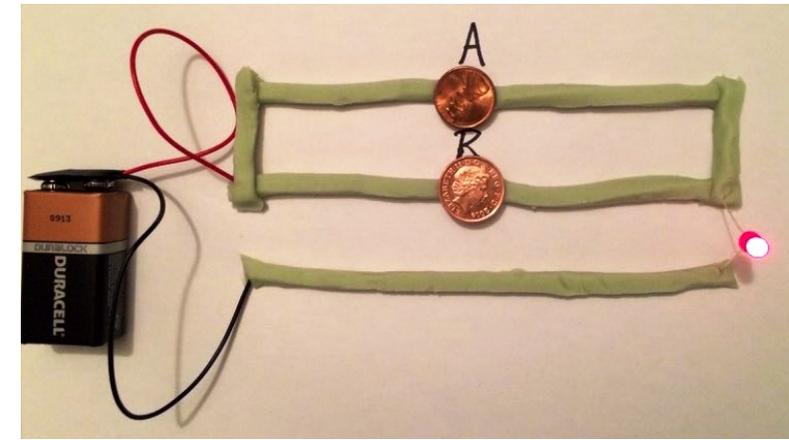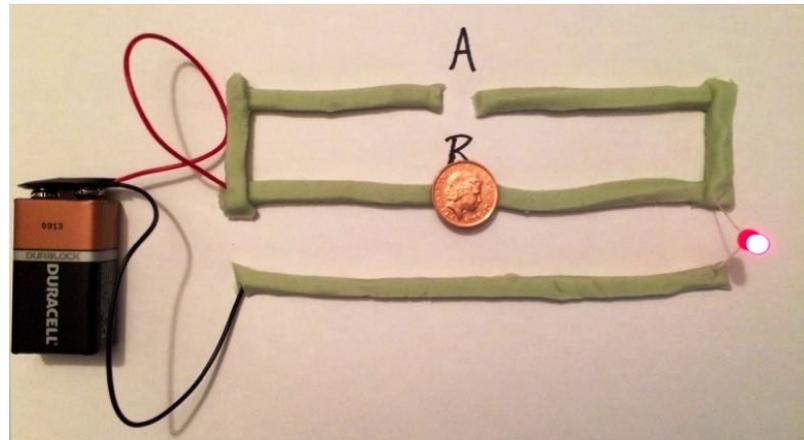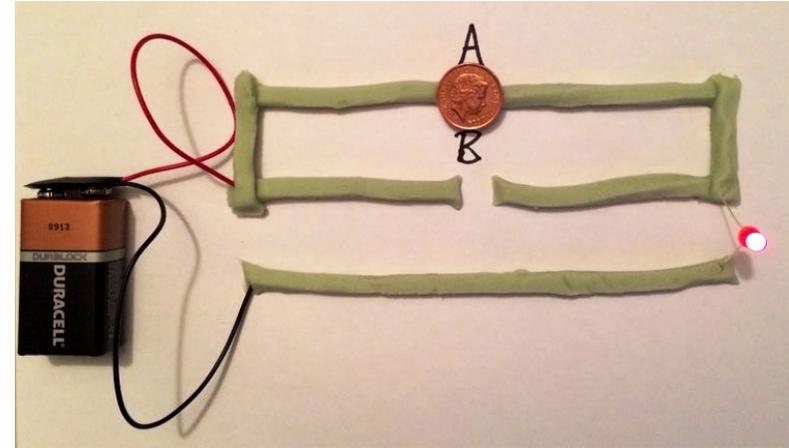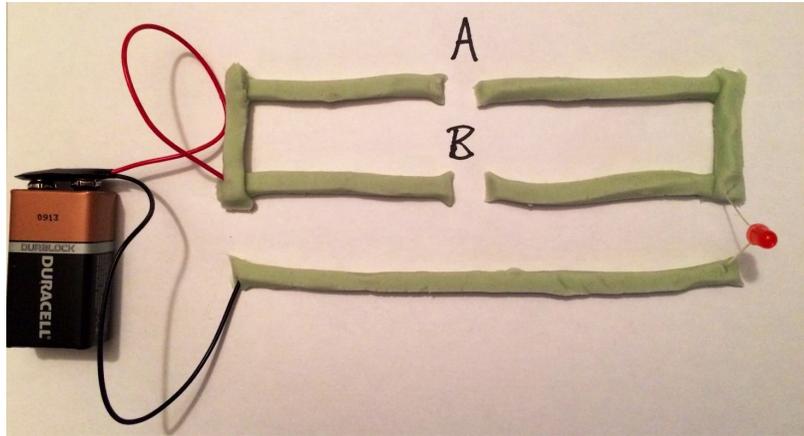

Truth table: A or B

A	B	$A \vee B$
0	0	0
0	1	1
1	0	1
1	1	1

Third Challenge

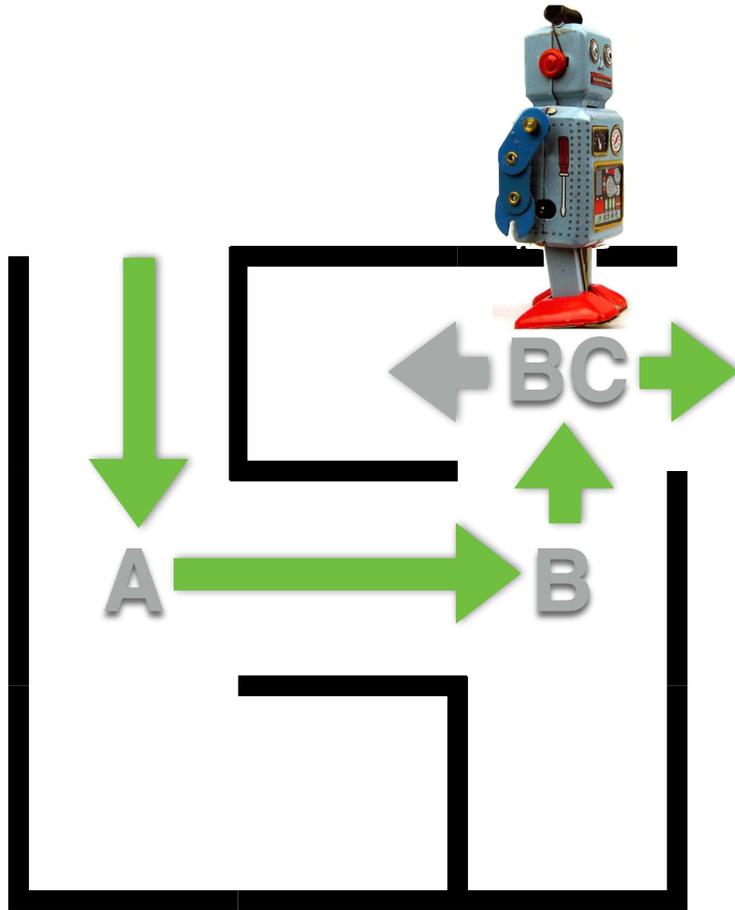


Turn left if
(A or B) and \bar{C}





- At the third junction the robot sees the sign 'BC' on the wall.
- Whereas before B switches the LED ON, in conjunction with C it must be OFF.

Logical AND

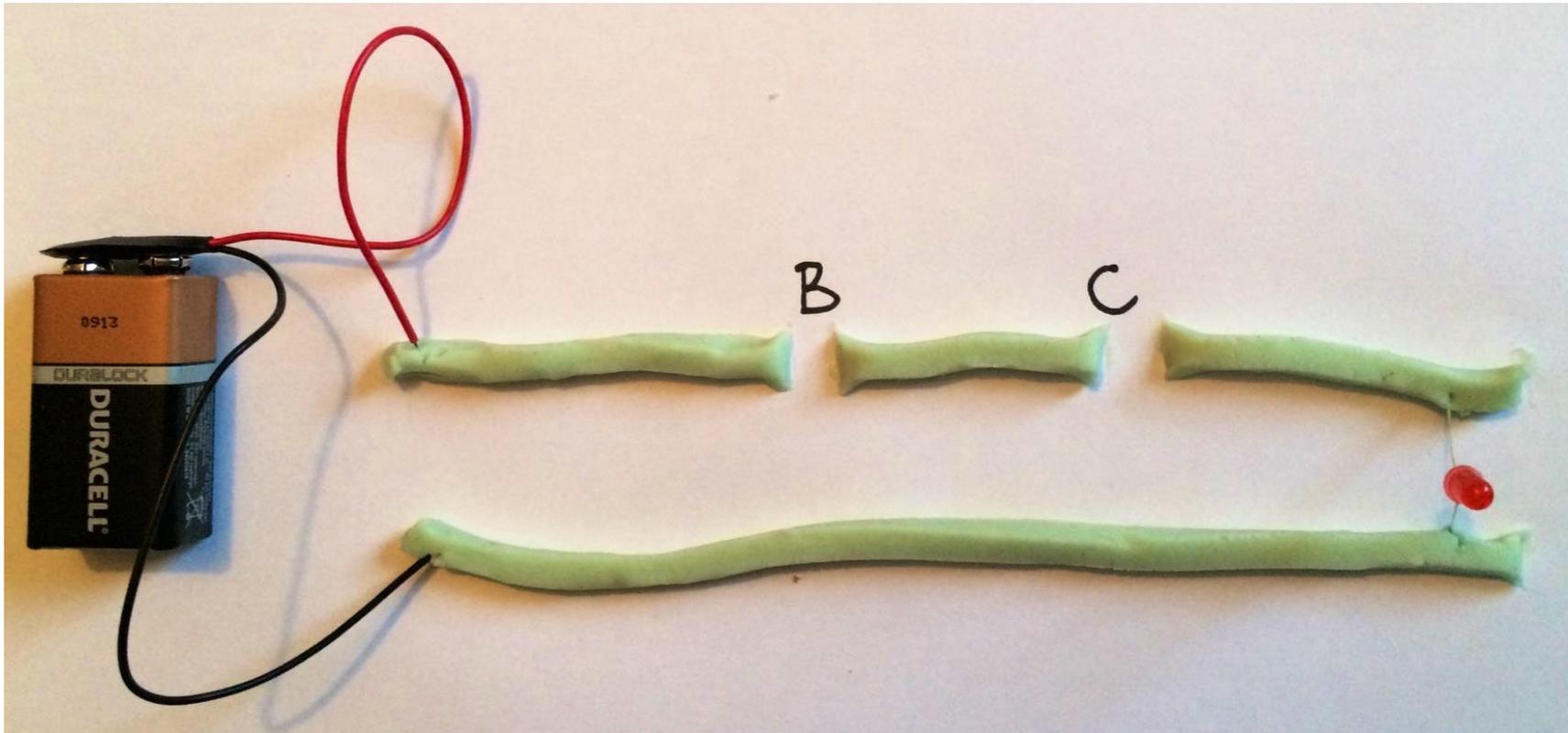- First of all - look at B AND C.
- The switches B, C are in series.





B and C

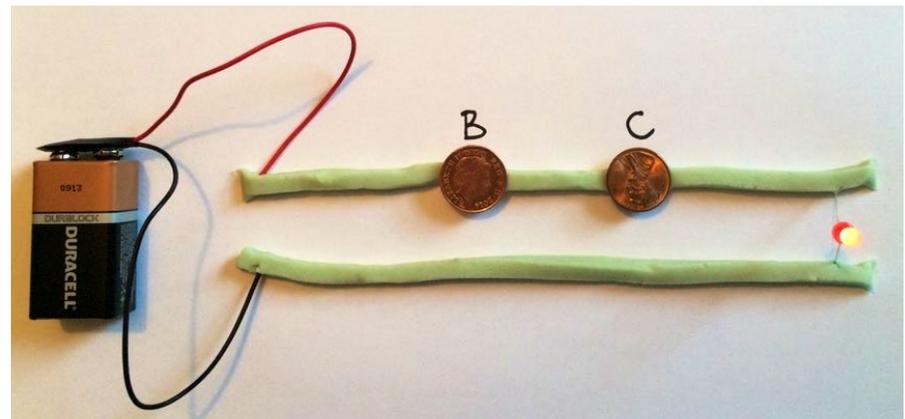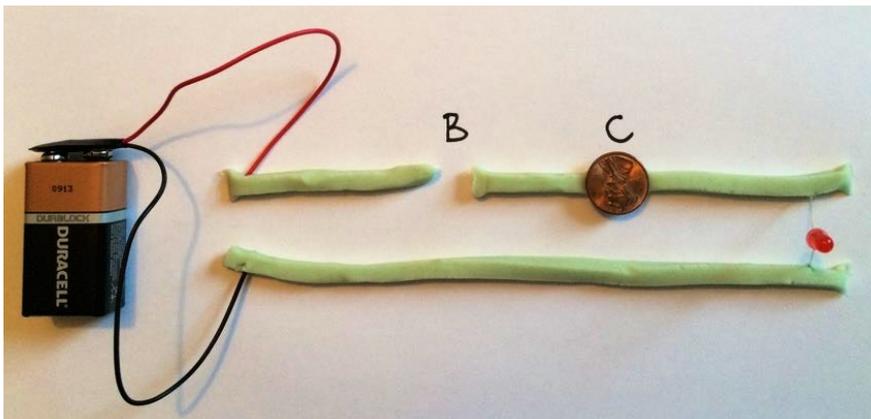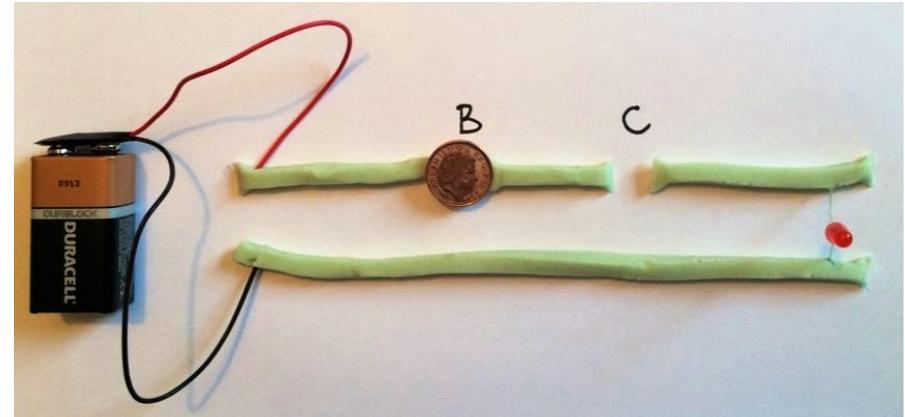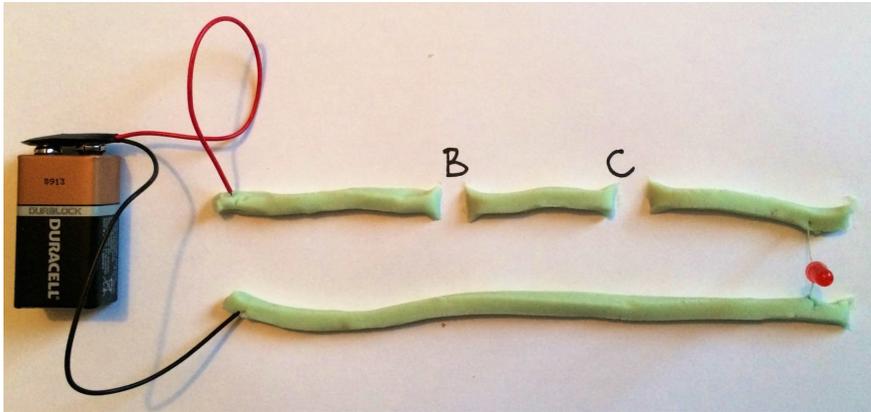

Truth table: A and B

B	C	$B \wedge C$
0	0	0
0	1	0
1	0	0
1	1	1

Not C, \bar{C}

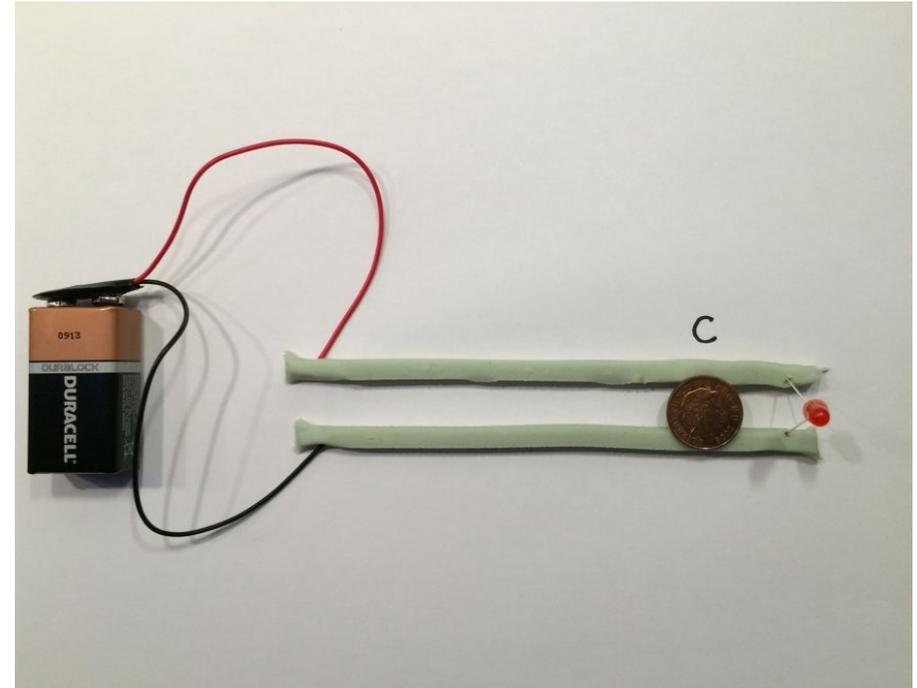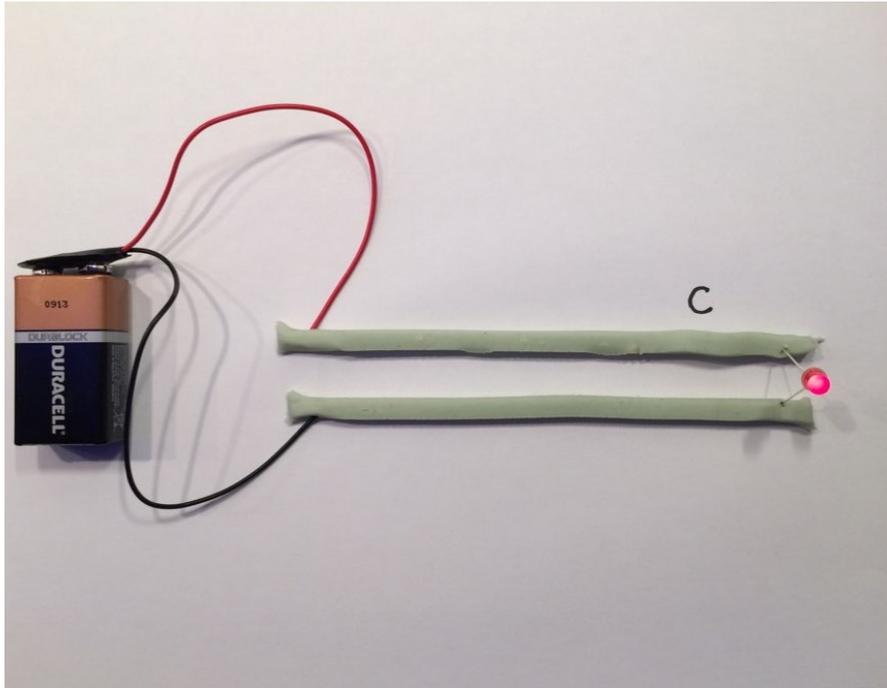


- Electricity tries to take the easy path. The penny is very conductive.
- Adding the penny pulls the circuit down to ground. The play dough is a resistor so this is not a short-circuit. **Never** short-circuit a battery.

Truth table: not C



c	\bar{c}
0	1
1	0

$(A \text{ or } B)$ and \bar{C}

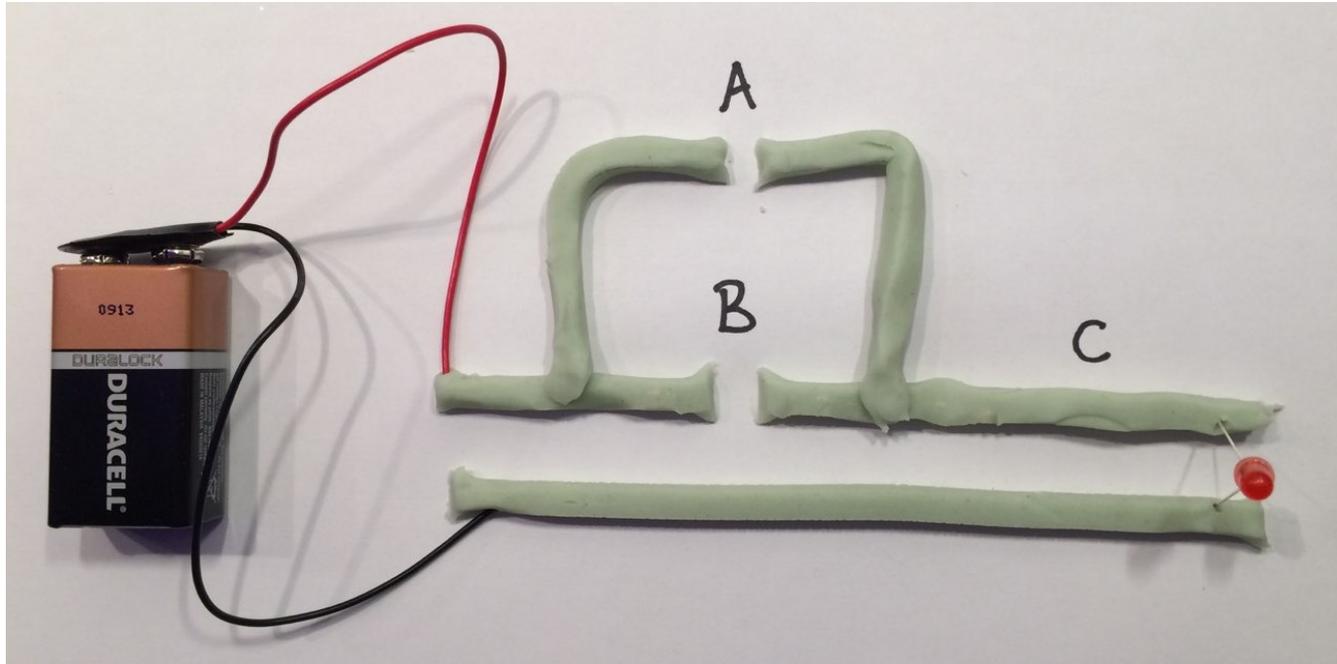





- This combines the parallel circuit $(A \text{ or } B)$ with the negation (not) of C .

(A or B) and \bar{C}

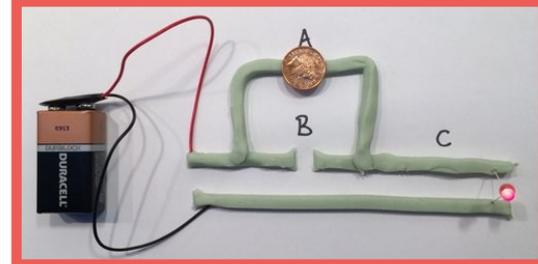
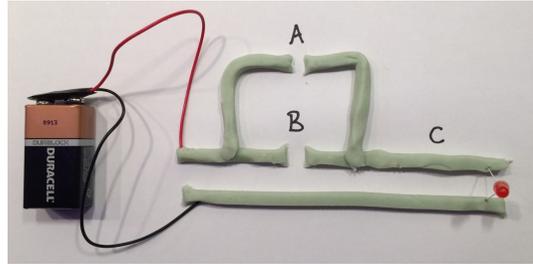


Turn left at the 1st junction.

Turn left at the 2nd junction.

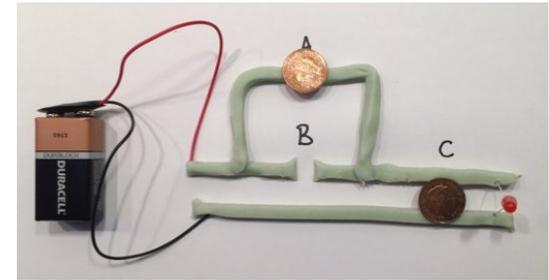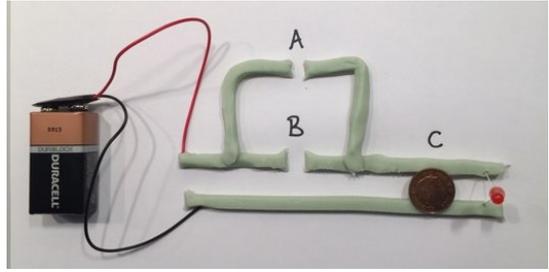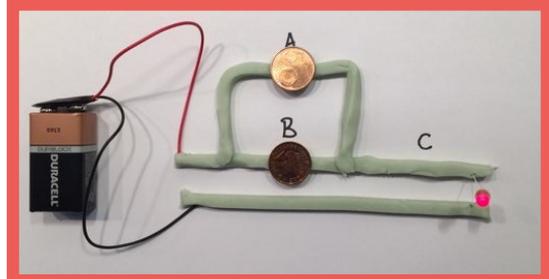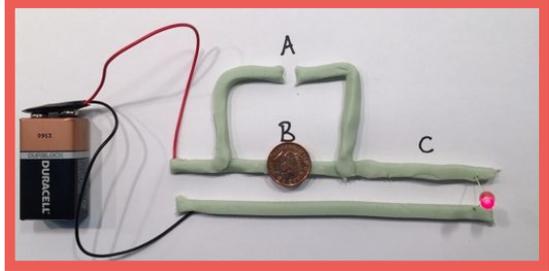

Turn right at the 3rd junction.

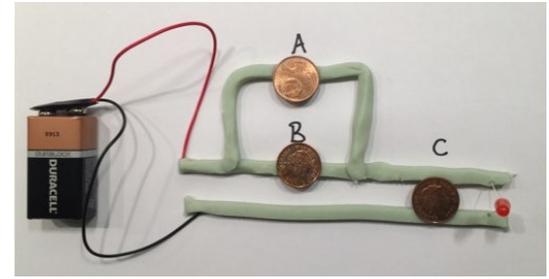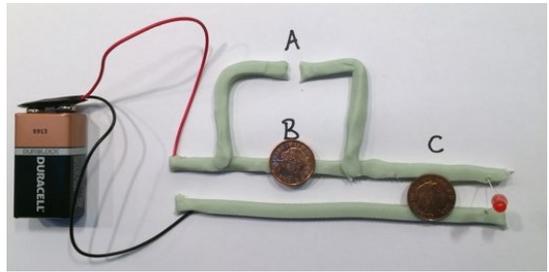

Truth table: (A or B) and \bar{C}

A	B	C	$A \vee B$	\bar{C}	$(A \vee B) \wedge \bar{C}$
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	1	1	1
0	1	1	1	0	0
1	0	0	1	1	1
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	0	0

- *Electrical logic circuits were first described by Claude Shannon, the creator of information theory, in 1937, "A Symbolic Analysis of Relay and Switching Circuits."*

<http://blog.stevebattle.me>

